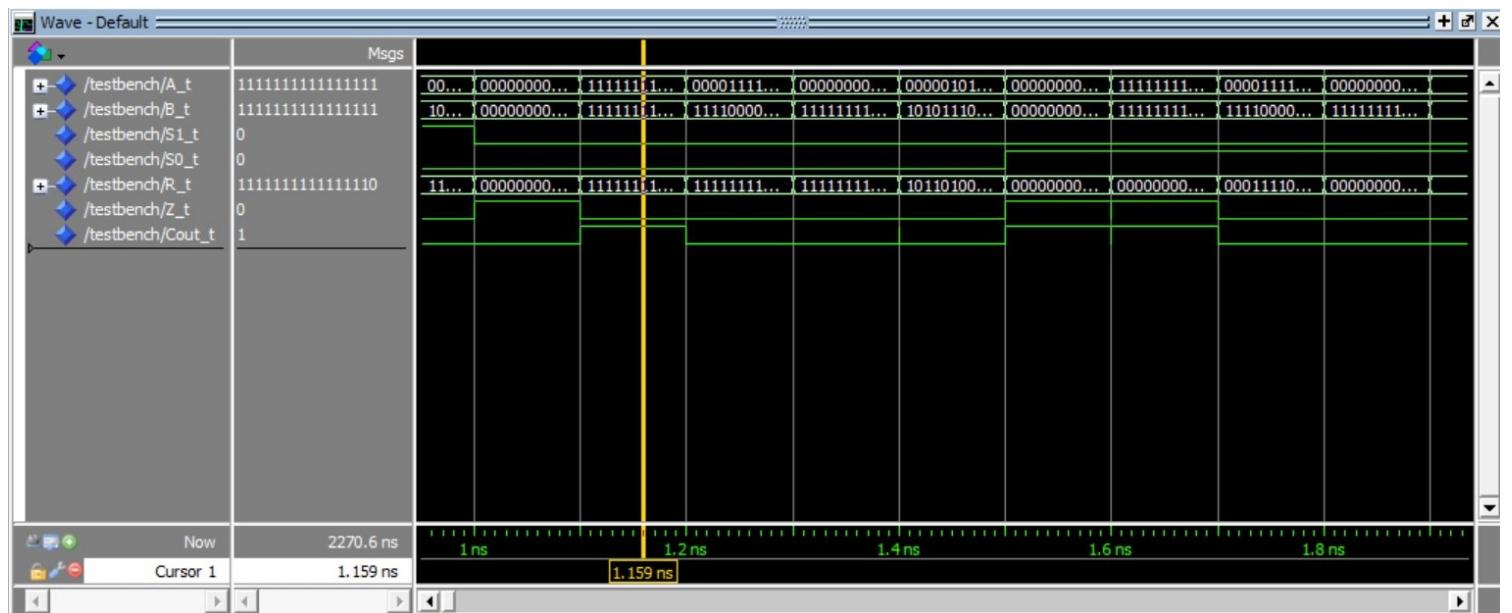



Name- Arif Ahmad
Roll no- 190110010
Electrical Engineering, BTech

Output Waveforms


1. Control Input = (00), Addition



2. Control Input = (01), Subtraction

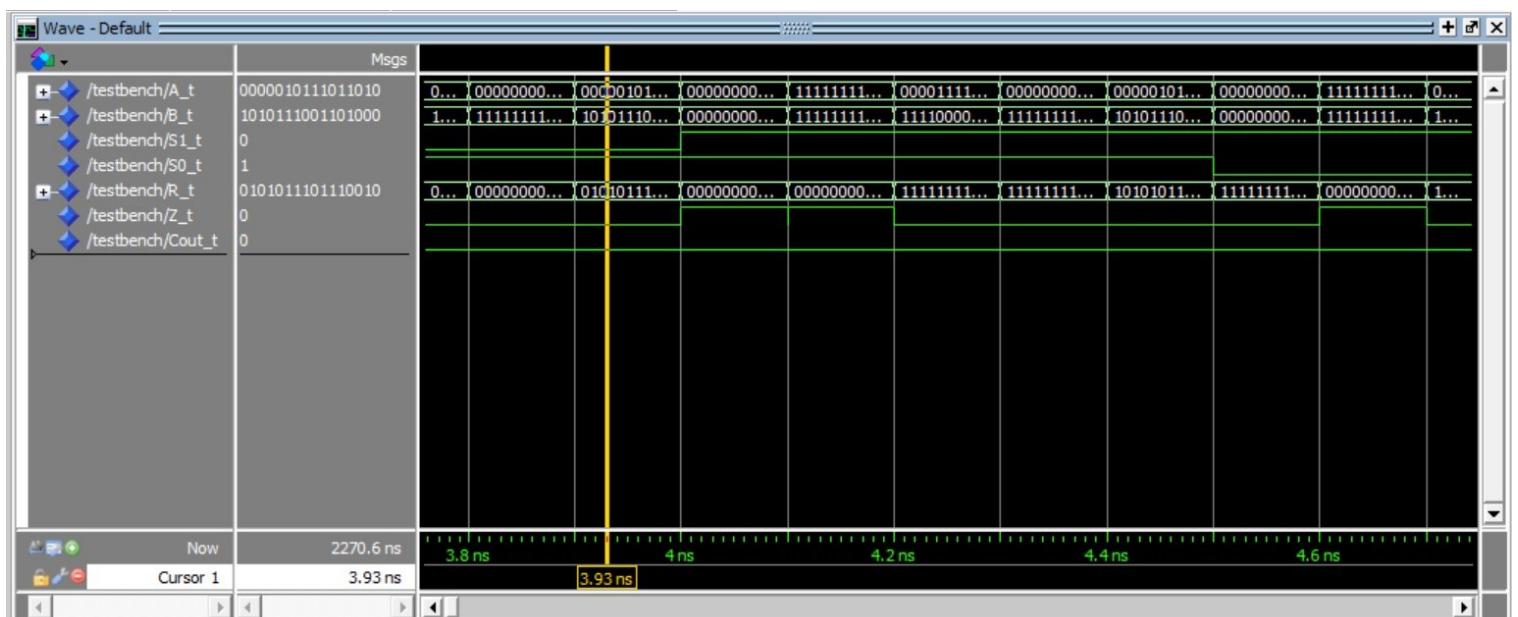

3. Control Input = (10), NAND operation

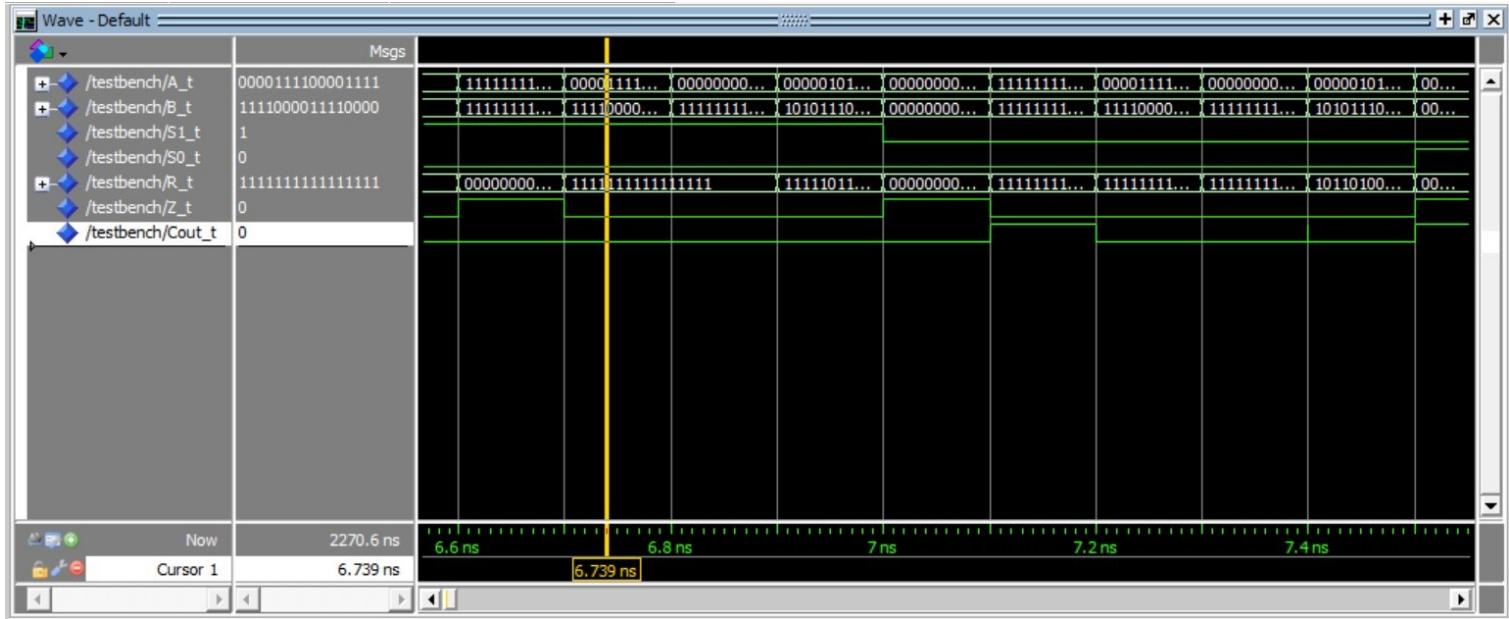

4. Control Input = (11), XOR operation

